



Fox Delta

Amateur Radio Projects & Kits

FC3 – 0718A

Schematic & Parts List: PIC18F4550 50/500MHZ Frequency Counter & RF Meter

FC3- 0718A 50/500MHZ Frequency Counter and RF Meter Kit Parts List:

Parts List For 2x16 LCD Version Kit:

Quantity	Part ID	Details
1	U1	PIC18F4550 DIP40 with FW2.04 pre-loaded
1	PCB	FD-FC3-0718A
1	IC Socket	40 PIN DIP
1	U3*	AD8307 SO8
1	U2	LM385-2.5V
1	U6	7805
1	U4*	MC12080 SO8
1	U5*	74VHC00 SO14
1	Q1	IRFD110
1	Q2*	ERA-3SM
1	Q3*	BFR93A
1	OSC	Oscillator 20MHZ Full size (DIP14)
1	P1	10K Preset
1	D1	1N4007 Diode
2	D2, D3	1N4148
1	RFC1*	22uH SMT
7	FBX1, 2, 3, 4, 5,6,7*	SMD FB Inductors
1	RFC2	82uH
1set	LCD Header	16PIN SIL 0.1INCH (Male + Ribbon) 8+8
1set	KB Header	8PIN SIL 0.1INCH (Male + Ribbon)
2	KB Buttons	12mm push Buttons
2	LED	3MM RED, GREEN
1	KB PCB	FC3-0915-1 or FC3-0718-1
1	J3	BNC R/A Connector
1	RLY	OEN42 12V 1CO Relay
1	LCD	2x16 LCD with BL
1	J2	USB Connector
1	J1	DC Connector
1	Case	Free powder coated metal case.
1	Set	LCD and KB mounting hardware

Parts marked with * are SMD and are pre-soldered for kits

Resistors – All 1/4W 5% unless specified

Quantity	Part ID	Details
3	R1, 2, 3	18 ohms
2	R4, 5	100 ohms
1	R23	2.2 ohms
1	R6	470K
1	R7	10
1	R8	100K
1	R9	820
1	R10	150
2	R11, 19	750K
2	R14, 33	470
1	R16	1.5K
1	R12	820K
1	R18	680K
2	R13, 17	220
3	C29, 30, 34	10K
2	R25, 32	1K
2	R20, 31	4.7K
1	R24	2.2K
2	R21, 22	22 Ohms
1	R35	3.3K
1	R15	33 ohms


Capacitors:

Quantity	Part ID	Details
5	C4, 6, 25, 17, 32	0.1uF Ploy
12	C5, 2, 10, 11, 14, 1, 15, 16, 20, 21, 29, 30	0.01uF Poly
11	C3, 7, 8, 9, 12, 13, 22, 19, 26, 27, 31	1uF Tantalum
1	C18	0.47uf
2	C23, 24	27pf Ceramic

Not included in this 2x16 LCD version kit:


**TFT Version Specific parts: TFT1, C28, FBX8, R26, R27, R28, 2PIN Headers
TFT-EN and BOOT.**

FC3-0718A CPU Schematic:

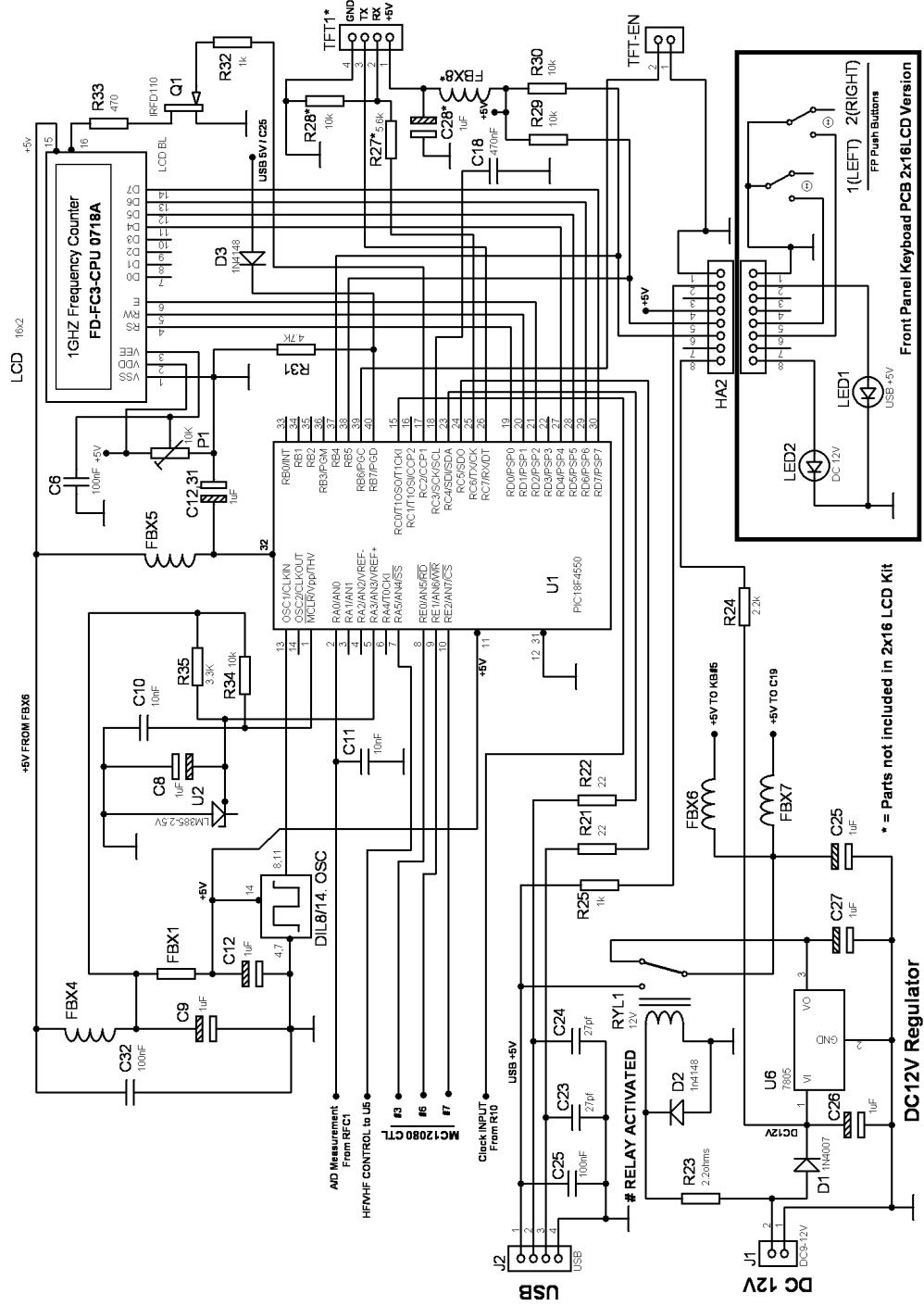


Project & Design by: Antonio Alfinito / I2TZK, Dinesh Gajjar / VU2FD, Frank Dziurda / K7SFN
Fox Delta FC3-0718A PART-1 <http://www.foxdelta.com> Supports 2X16 LCD and TFT

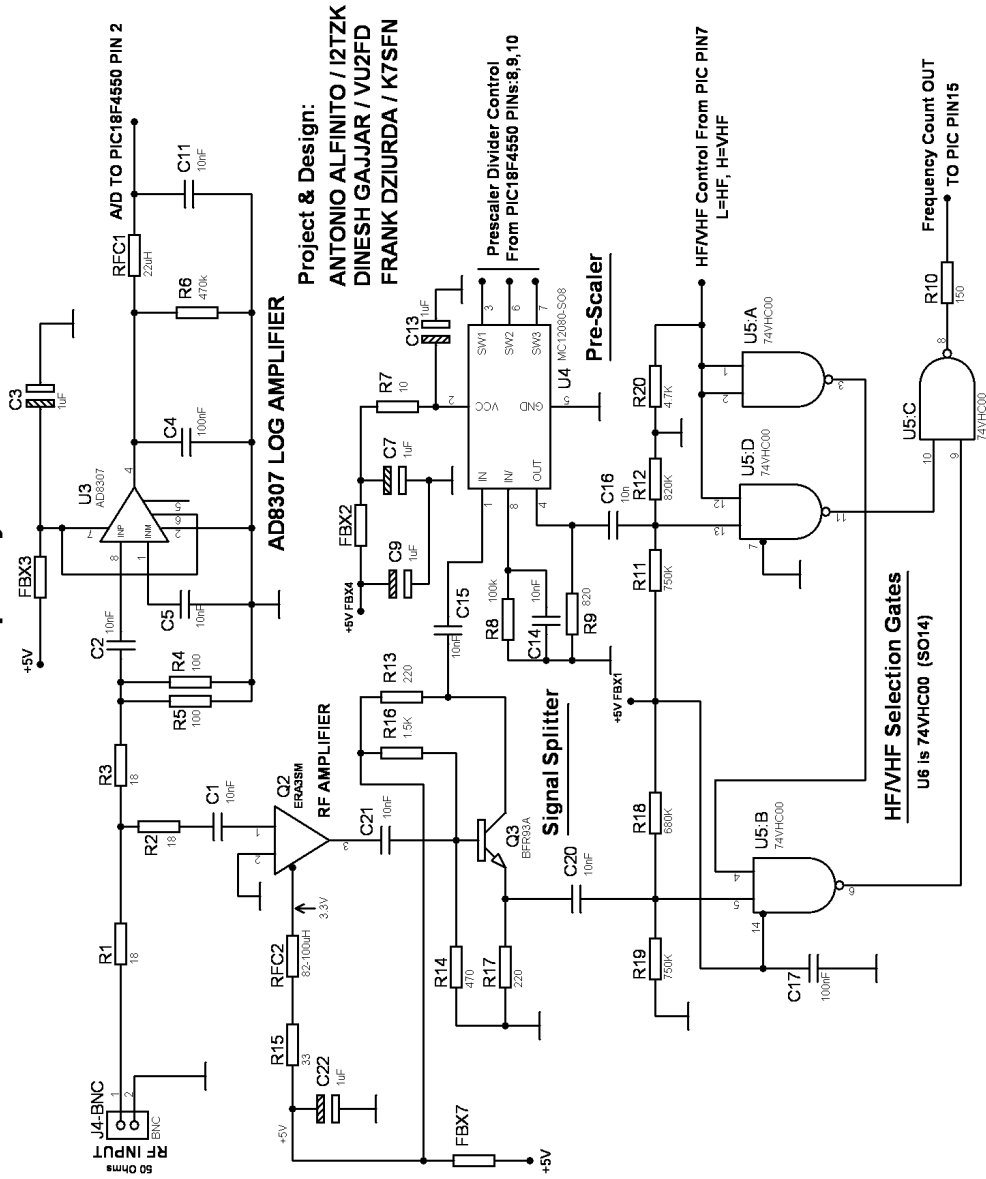FC3-0718A 500MHZ LCD Frequency Counter & RF Meter




<http://www.foxdelta.com> Schematic: FC3-INPUT-0718A PART-2

FC3-0718A PCB TOP SILK:

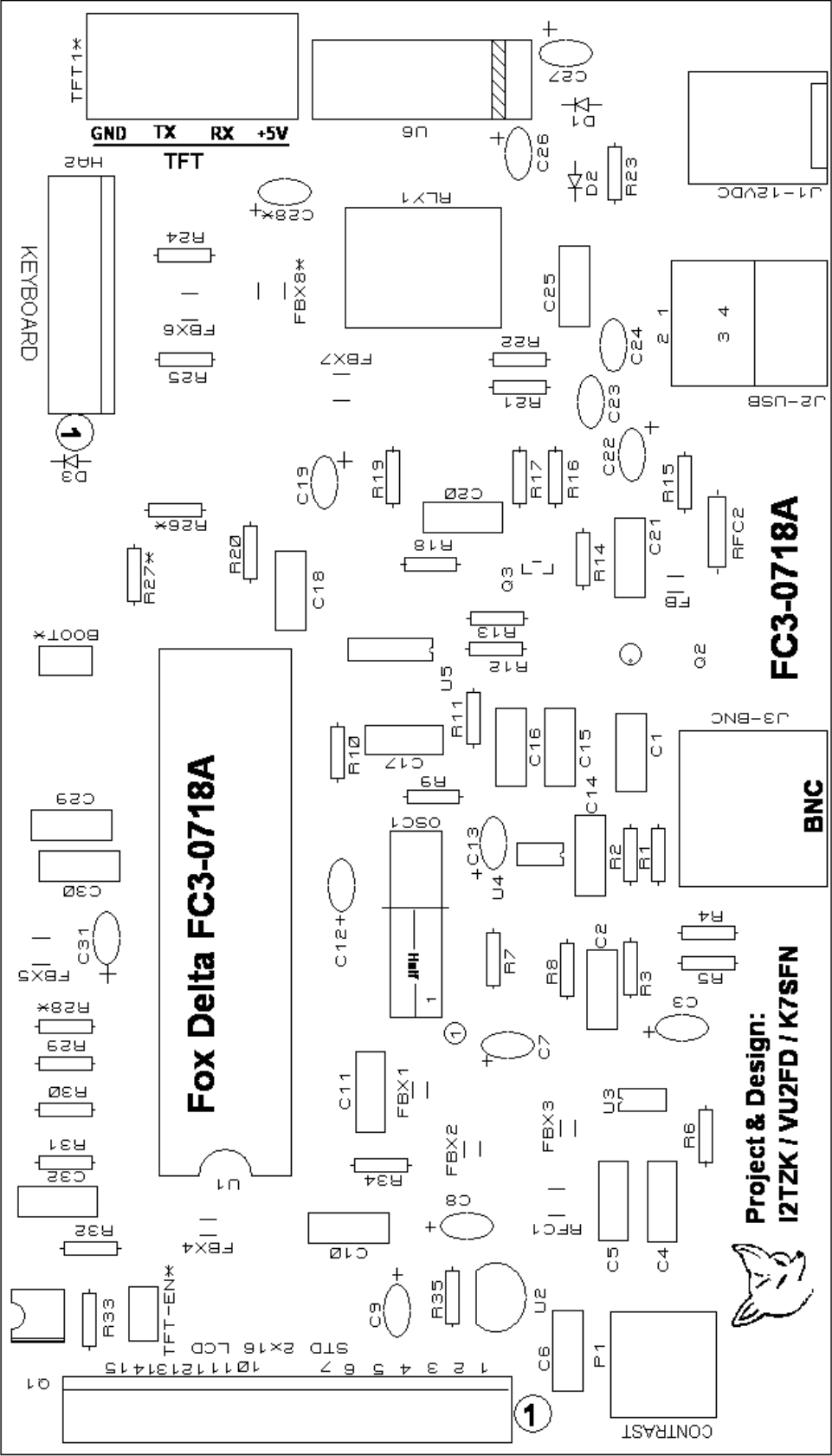

FC3- 0915-1 / 0718-1 Key Board PCB SILK:

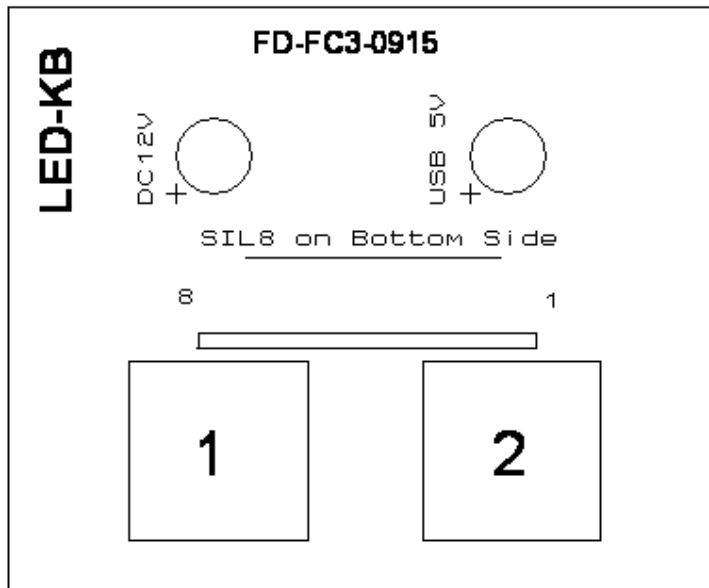

Notes:

1. **SMT Parts:** AD8307, MC12080, ERA3SM/74HC, BFR and Ferrite Bead are pre-soldered on PCB
2. PCB Rev 0718 is exactly same as 0915 except that Ferrite Beads are SMD and are pre-soldered for kits. This revision also support 3.2" TFT with change in PIOC Code.
3. **Ensure** that you pay attention to OSCILLATOR **orientation**. OSC pin 1 is marked by a dot and by way of square edge on body.
4. **Q1 is IRFD110.** Make sure that two pins which are together, goes to pads marked by black line on SILK.
5. **LCD headers:** 2 X 8SIL headers are Pre-soldered on main PCB for kits. 2 set of 8PIN ribbon cables are supplied. Connect ribbon cables for each socket marked as "1" and "2".
6. **Keyboard:** 8PIN SIL header is pre-soldered on main PCB and KB PCB for kits.

73s

Dinesh Gajjar
18th Sept 2019

For more details on this project please visit <http://www.foxdelta.com>